

# **Binary Adders**

*By*  
*P. K. Roy*

# Half Adder

- Addition of 2 bits only.
- No requirement of initial carry.



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Sum represents Ex-OR gate and Carry represents AND gate.

$$\text{Sum} = \overline{A} \cdot B + A \cdot \overline{B}$$

$$\text{Carry} = A \cdot B$$

Cntd...

  

# Full Adder


- Addition of 3 bits only.
- Requires an initial carry.

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$\text{Sum} = \overline{A} \bullet \overline{B} \bullet C + \overline{A} \bullet B \bullet \overline{C} + A \bullet \overline{B} \bullet \overline{C} + A \bullet B \bullet C$$

$$\text{Carry} = A \bullet B + A \bullet C + B \bullet C$$

Cntd...

 

# Designing FA Using HA

 

*Home Work: HS & FS*

# When FA Behaves Like HA?

$$\text{Sum} = \overline{A} \bullet \overline{B} \bullet C + \overline{A} \bullet B \bullet \overline{C} + A \bullet \overline{B} \bullet \overline{C} + A \bullet B \bullet C$$

$$\text{Carry} = A \bullet B + A \bullet C + B \bullet C$$


Suppose we let the carry-in  $C = 0$ . Then  $\overline{C} = 1$ .  
What we have then is as follows.

$$\begin{aligned} \text{Sum} &= \overline{A} \bullet \overline{B} \bullet 0 + \overline{A} \bullet B \bullet 1 + A \bullet \overline{B} \bullet 1 + A \bullet B \bullet 0 \\ &= \overline{A} \bullet B + A \bullet \overline{B} \end{aligned}$$

$$\begin{aligned} \text{Carry} &= A \bullet B + A \bullet 0 + B \bullet 0 \\ &= A \bullet B \end{aligned}$$
 
# The Full-Adder and Half-Adder as Circuit Elements

- Each circuit is denoted as a simple box with inputs and outputs.




- (a) full-adder with carry-in
- (b) full-adder acting as a half-adder
- (c) half-adder with no carry-in



# Serial Adder

For addition of 2 binary numbers.

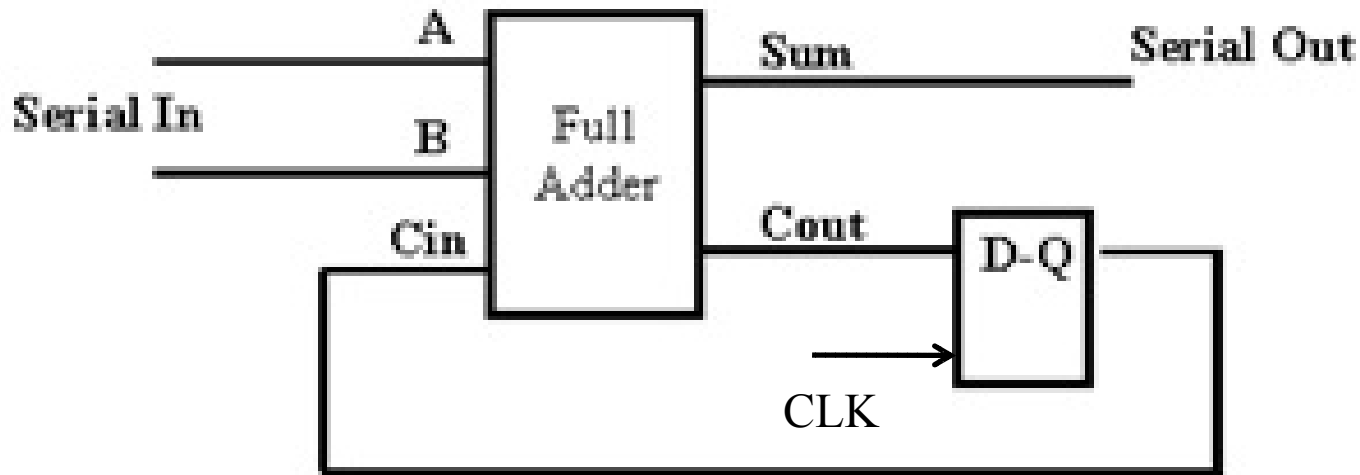

## *Disadvantage:*

1. Addition process is performed by bit-by-bit.
2. Time required for addition depends on number of bits (for n no. of bits it will be n clock cycles).

# Parallel Adder


- For addition of 2 binary numbers.
- All bits are added concurrently.
- Time required does not depend on the number of bits.

Are of 2 types –

1. Carry Propagate Adder (CPA) or Ripple Carry Adder
2. Carry Look-Ahead Adder

 
# Ripple Carry Adder or CPA

- *Propagating the Carry Bits* – carry-out from one stage is carried into the next stage.



# Cntd...

Considering both A & B are of 4bits

 

*4 – bit Ripple Carry Adder*

## *Disadvantage:*

1. Each FA has to wait for its Carry-in generated from the previous FA (except the initial one. )
2. **Max. Delay** –  $n\Delta$  for n-bit nos.

# Carry Look-Ahead Adder

A	B	C	Sum	Carry	
0	0	0	0	0	} <i>No Generate , No Propagate</i>
0	0	1	1	0	
0	1	0	1	0	} <i>Carry Propagate</i>
0	1	1	0	1	
1	0	0	1	0	
1	0	1	0	1	
1	1	0	0	1	} <i>Carry Generate</i>
1	1	1	1	1	


# Cntd...

- A carry signal will be generated in two cases:
  - (1) when both bits  $A^i$  and  $B^i$  are 1, or
  - (2) when one of the two bits is 1 and the carry-in (carry of the previous stage) is 1.

Hence,

$$P_i = A_i \oplus B_i \dots\dots\dots(1)$$

$$G_i = A_i B_i \dots\dots\dots(2)$$

 

# Cntd...

The output sum and carry can be defined as :

$$S_i = P_i \oplus C_i \dots\dots\dots(3)$$

$$C_{i+1} = G_i + P_i C_i \dots\dots\dots(4)$$

$G_i$  is known as the *carry Generate* signal since a carry ( $C_{i+1}$ ) is generated whenever  $G_i = 1$ , regardless of the input carry ( $C_i$ ).

$P_i$  is known as the *carry propagate* signal since whenever  $P_i = 1$ , the input carry is propagated to the output carry, i.e.,  $C_{i+1} = C_i$  (note that whenever  $P_i = 1$ ,  $G_i = 0$ ).

# Cntd...

Considering 4-bit numbers –

The Boolean expression of the carry outputs of various stages can be written as follows:

$$C_1 = G_0 + P_0C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1C_1 = G_1 + P_1(G_0 + P_0C_0) \\ &= G_1 + P_1G_0 + P_1P_0C_0 \end{aligned}$$


$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

$$\begin{aligned} C_4 &= G_3 + P_3C_3 \\ &= G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0C_0 \end{aligned}$$

**Conclusion:** All of the Carry<sub>out</sub> signals can be derived from the initial Carry<sub>in</sub> signal only.



Cntd...

 

**Max. Delay** –  $6\Delta$  for n-bit nos. : For  $G_i$  &  $P_i \Rightarrow \Delta$  ;  
 For  $C_i \Rightarrow 2\Delta$  ; for  $S_i \Rightarrow 3\Delta$


**HW:** 1. Design a 16-bit CPA using 4-bit CPAs

2. Derive the carry generate-propagate expressions for 8-bit CLA

# 4-Bit Binary Incrementer Unit


$$\begin{array}{rcccc} c & c & c & c & \\ & a_3 & a_2 & a_1 & a_0 \\ + & & & & 1 \\ \hline C & S_3 & S_2 & S_1 & S_0 \end{array}$$

Addition of 1 with the actual number

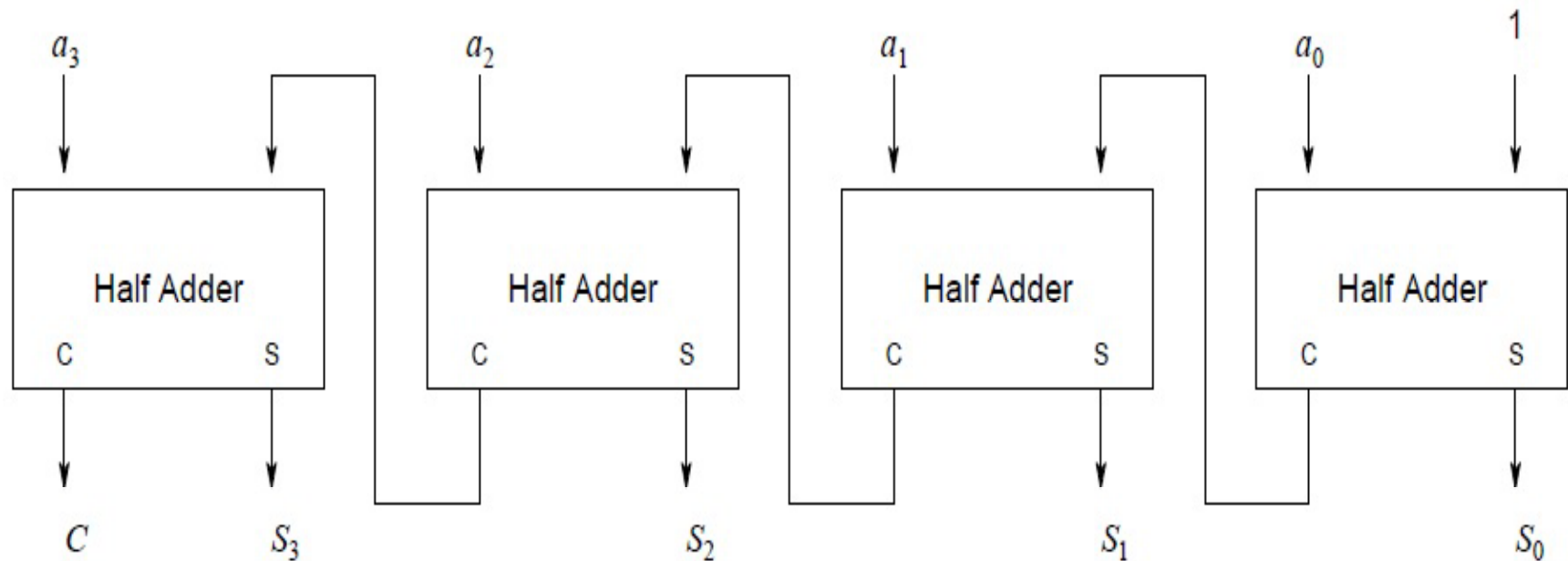

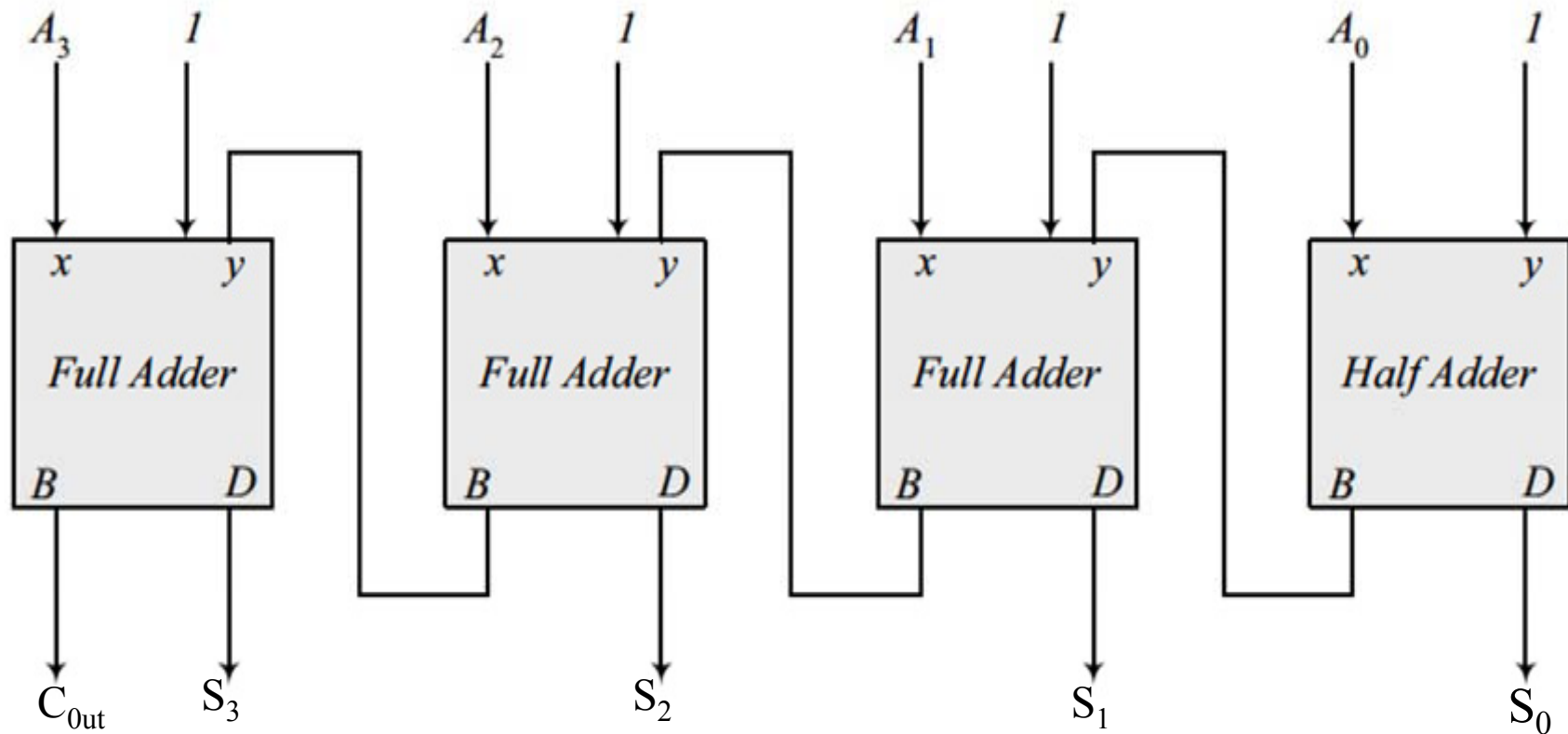
# 4-Bit Binary Decrementer Unit

$$A_3A_2A_1A_0 - 1 \Rightarrow A_3A_2A_1A_0 + 1111$$


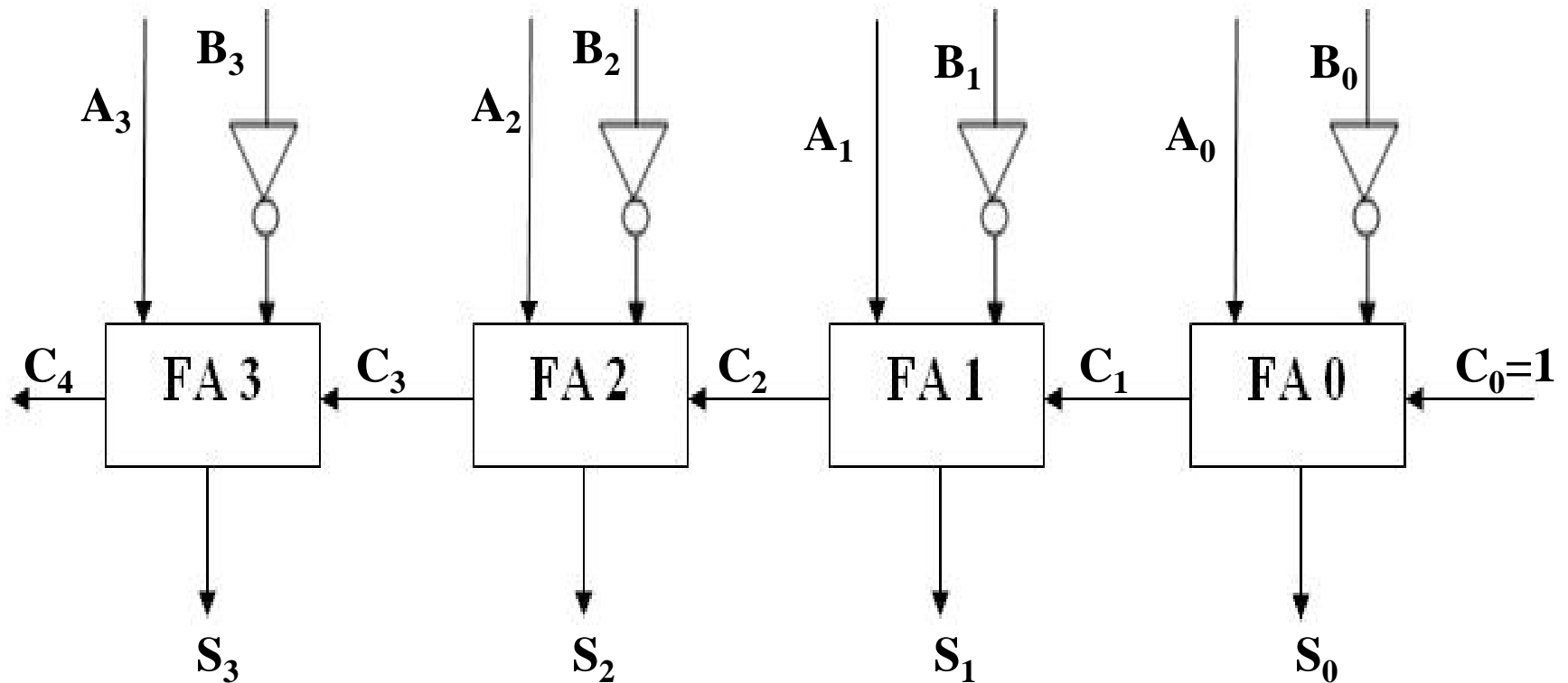
# 4-bit Parallel Subtractor


$A - B \Rightarrow A + \text{complement of } B + 1$


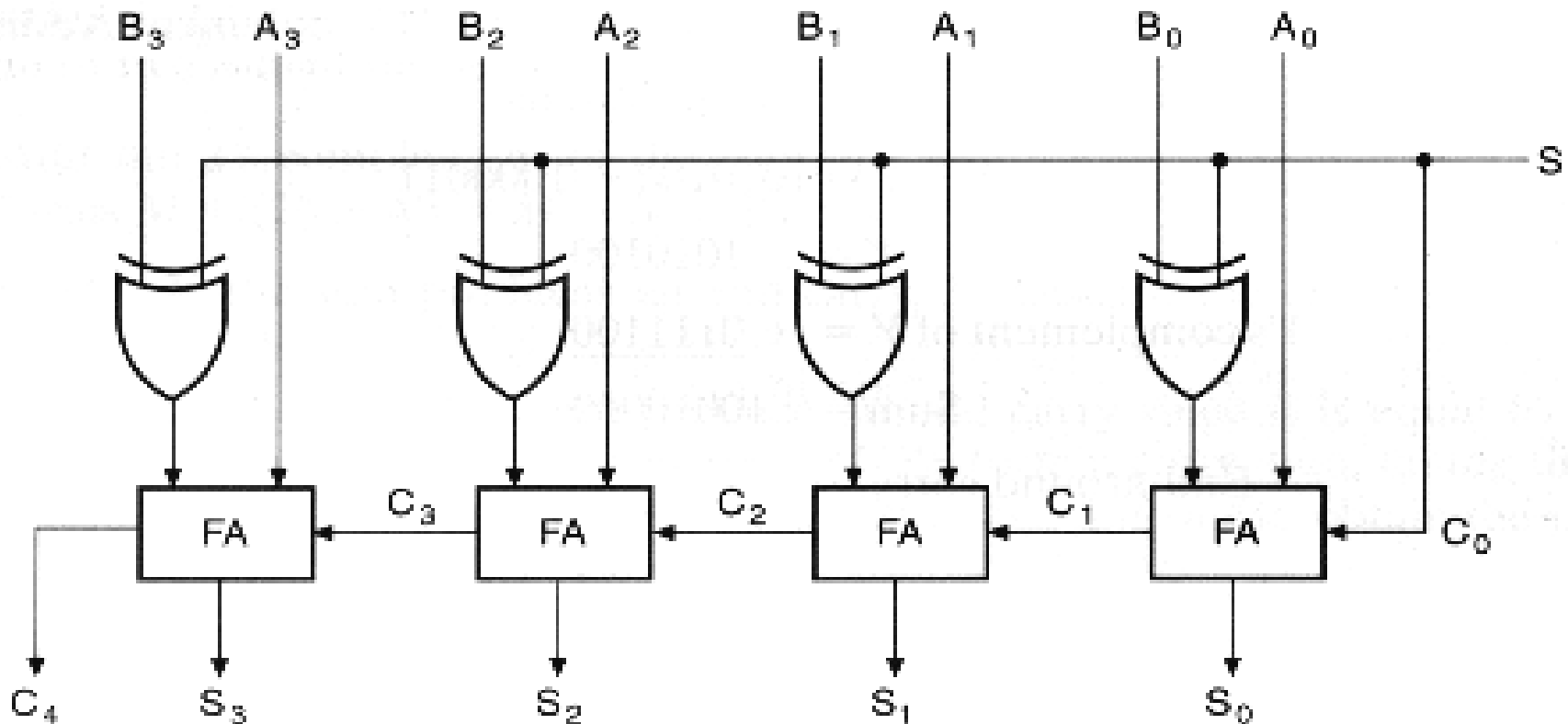
# 4-bit Adder/Subtractor Composite Unit

$S=1 \Rightarrow$  Subtraction  $\Rightarrow A + \text{complement of } B + 1 \Rightarrow A - B$

$S=0 \Rightarrow$  Addition  $\Rightarrow A + B + 0 \Rightarrow A + B$





1. If both of the inputs in CLA are 0, carry is –
  - a) generated
  - b) propagated
  - c) neither generated nor propagated
  - d) none of these
2. Basic FA performs addition of –
  - a) 2 bits
  - b) 3 bits
  - c) 4bits
  - d) 2 multi-bit numbers
3. FA is equivalent to HA only when carry-in is-
  - a) 0
  - b) 1
  - c) 2
  - d) 3
4. To add 2 n-bit nos. using parallel adder, the no. of clock cycle is –
  - a) 1
  - b) 2
  - c) n
  - d) 2n
5. To add 2 n-bit nos. in serial adder, the no. of clock cycle is –
  - a) 1
  - b) 2
  - c) n
  - d) 2n
6. To add 2 n-bit nos. using CPA ,the max. delay is –
  - a)  $\Delta$
  - b)  $2\Delta$
  - c)  $6\Delta$
  - d)  $n\Delta$
7. To add 2 n-bit nos. using CLA ,the max. delay is –
  - a)  $\Delta$
  - b)  $2\Delta$
  - c)  $6\Delta$
  - d)  $n\Delta$

8. Which one is faster than the others –

- a) Serial adder   b) CPA   c) CLA   d) Can't be determined

9. FA has ..... Outputs

- a) 1                  b) 2                  c) 3                  d) 4

10. HA has ..... Outputs

- a) 1                  b) 2                  c) 3                  d) 4

11. FA has ..... Inputs

- a) 1                  b) 2                  c) 3                  d) 4

12. HA has ..... Inputs

- a) 1                  b) 2                  c) 3                  d) 4

13. If both of the inputs in CLA are 1, carry is –

- a) generated                                  b) propagated  
c) neither generated nor propagated      d) none of these

14. If both of the inputs in CLA are different, carry is –

- a) generated                                  b) propagated  
c) neither generated nor propagated      d) none of these



15. The initial FA for n-bit CPA can be considered as an HA

- a) True                      b) False

16.  $C_{i+1} = C_i$  is equivalent to –

- a) generate              b) propagate              c) both              d) none

17.  $A_i B_i$  is equivalent to -

- a) generate              b) propagate              c) both              d) none

References:

1. Salivahanan
2. T. K. Ghosh

————— *Thank You* —————

*Thank You*