

Binary Multiplication & Division

By
P. K. Roy

Topics to be Covered


Binary Multiplication:

1. Sequential Multiplier for Unsigned Numbers
2. Booth's Multiplier for Signed Numbers


Binary Division:

1. Restoring Division Method for Unsigned Numbers
2. Non-Restoring Division Method for Unsigned Numbers


2x2 - Bits Array Multiplier

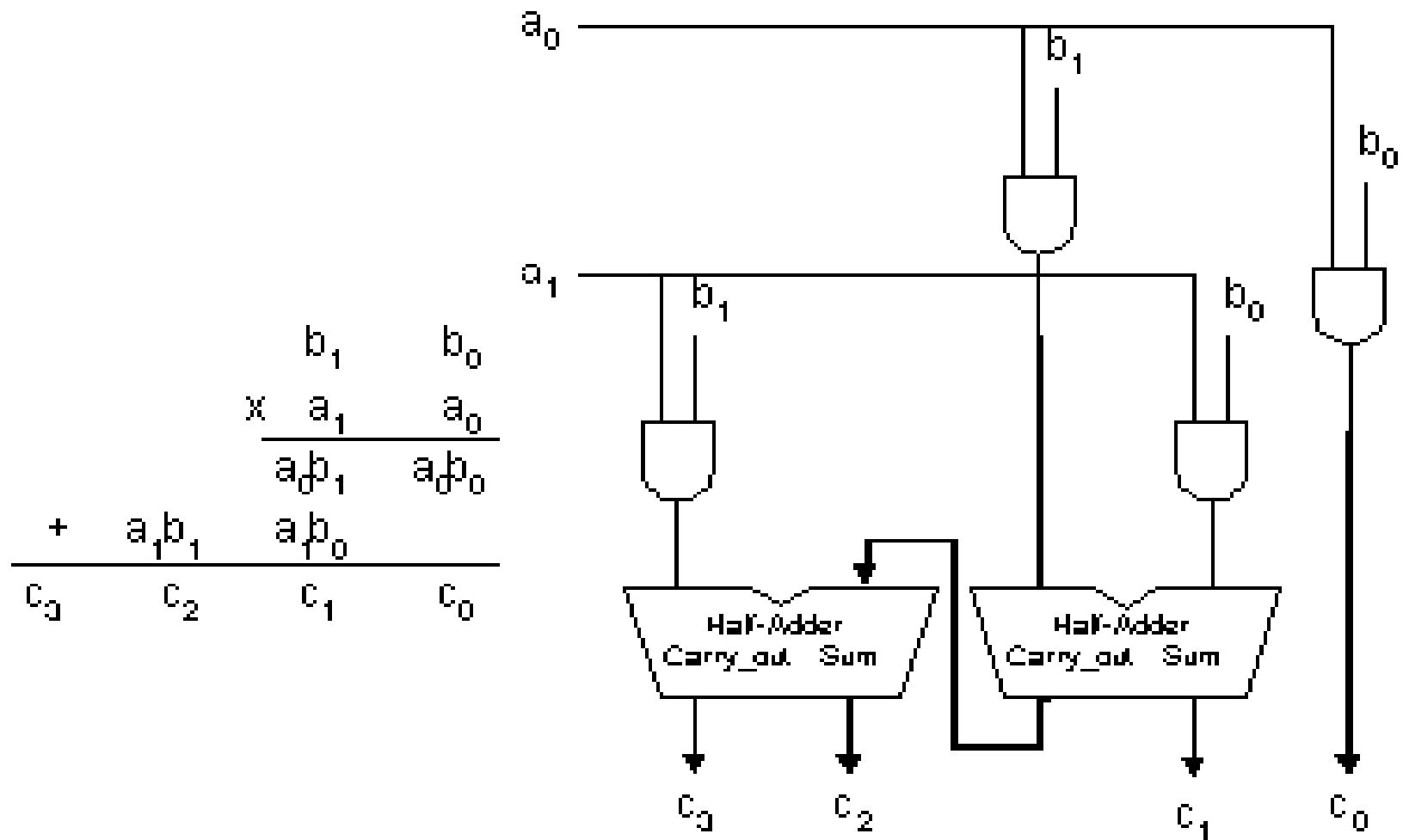


Sequential Multiplier

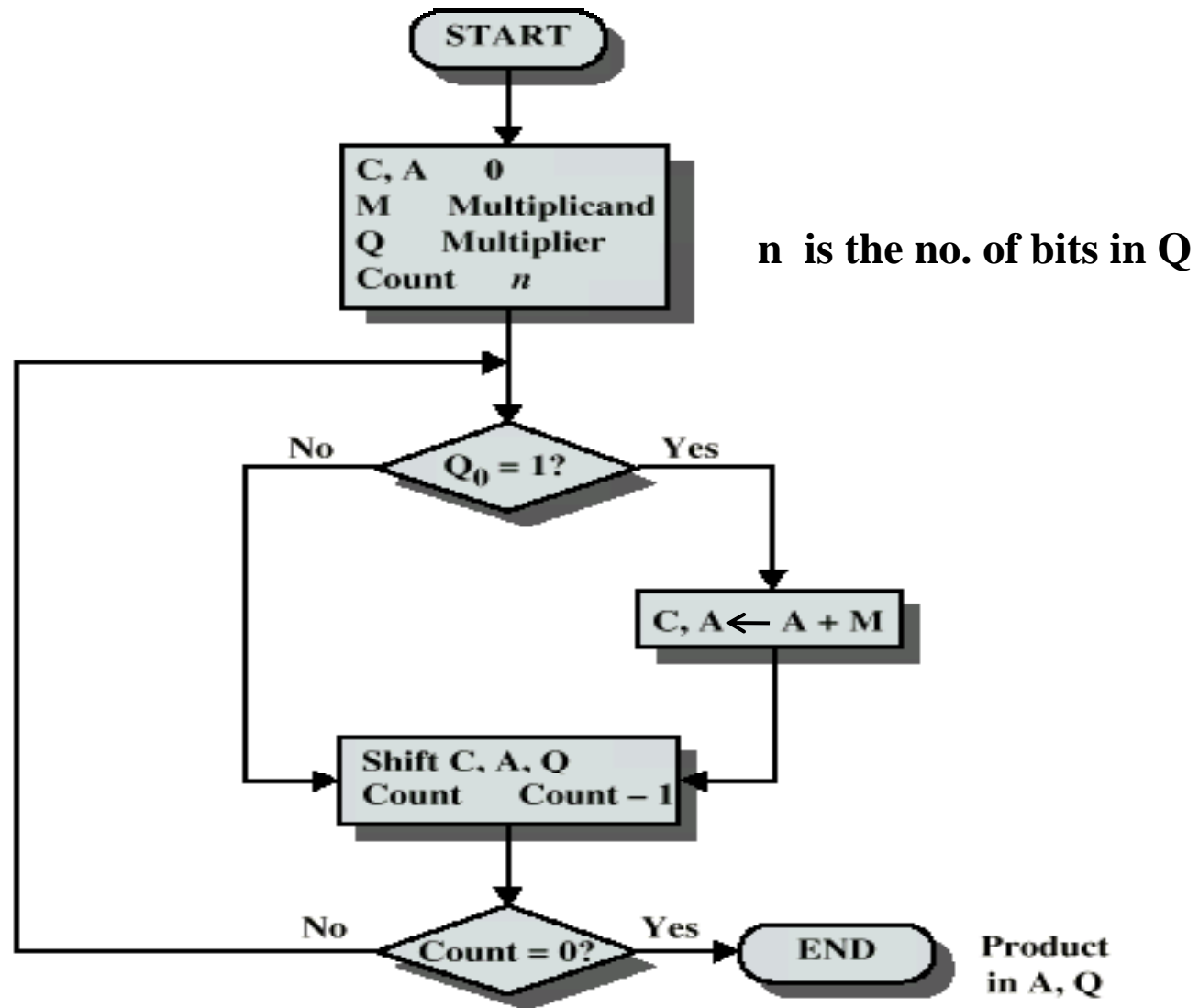


Booth's Multiplier

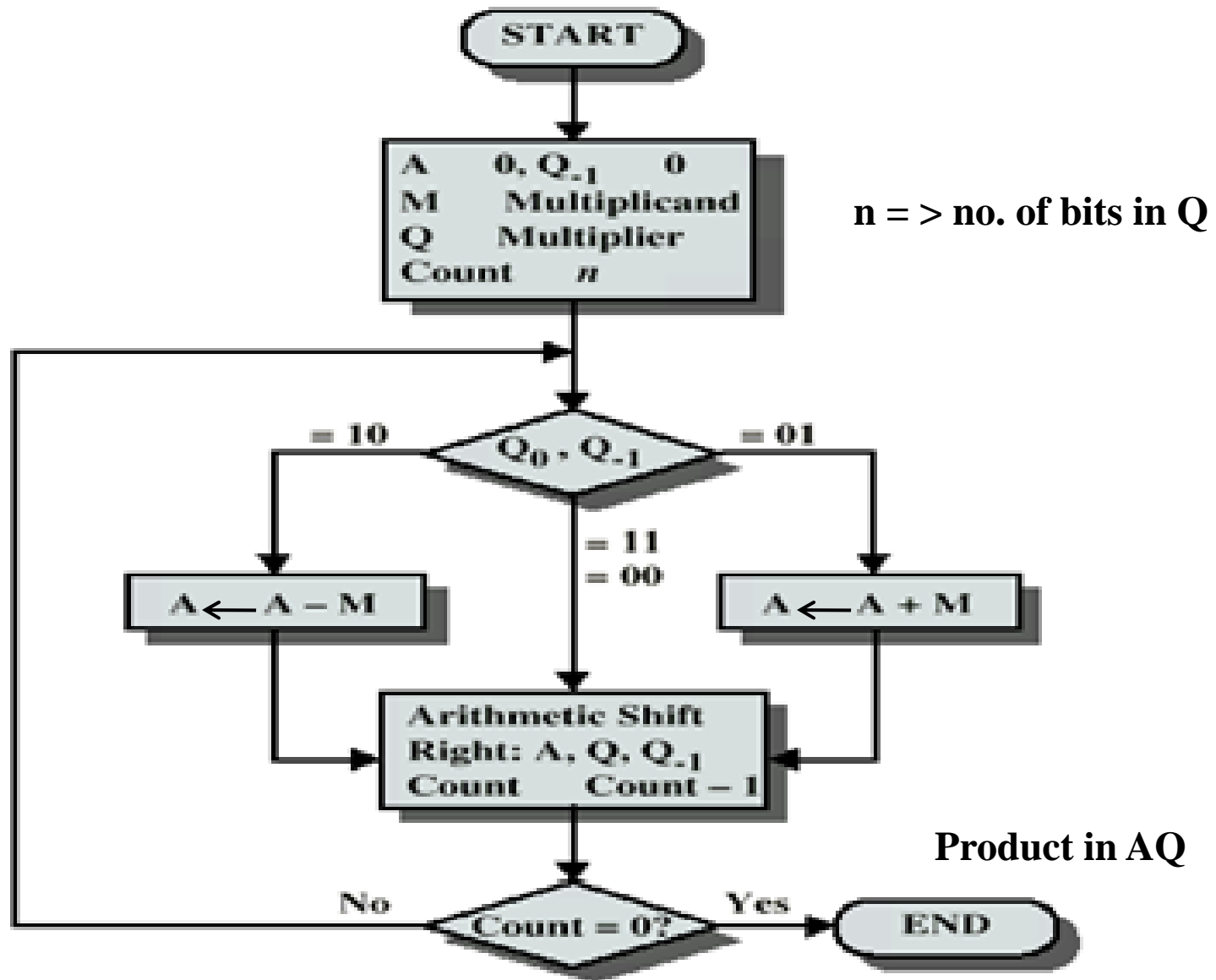

Restoring Division Method

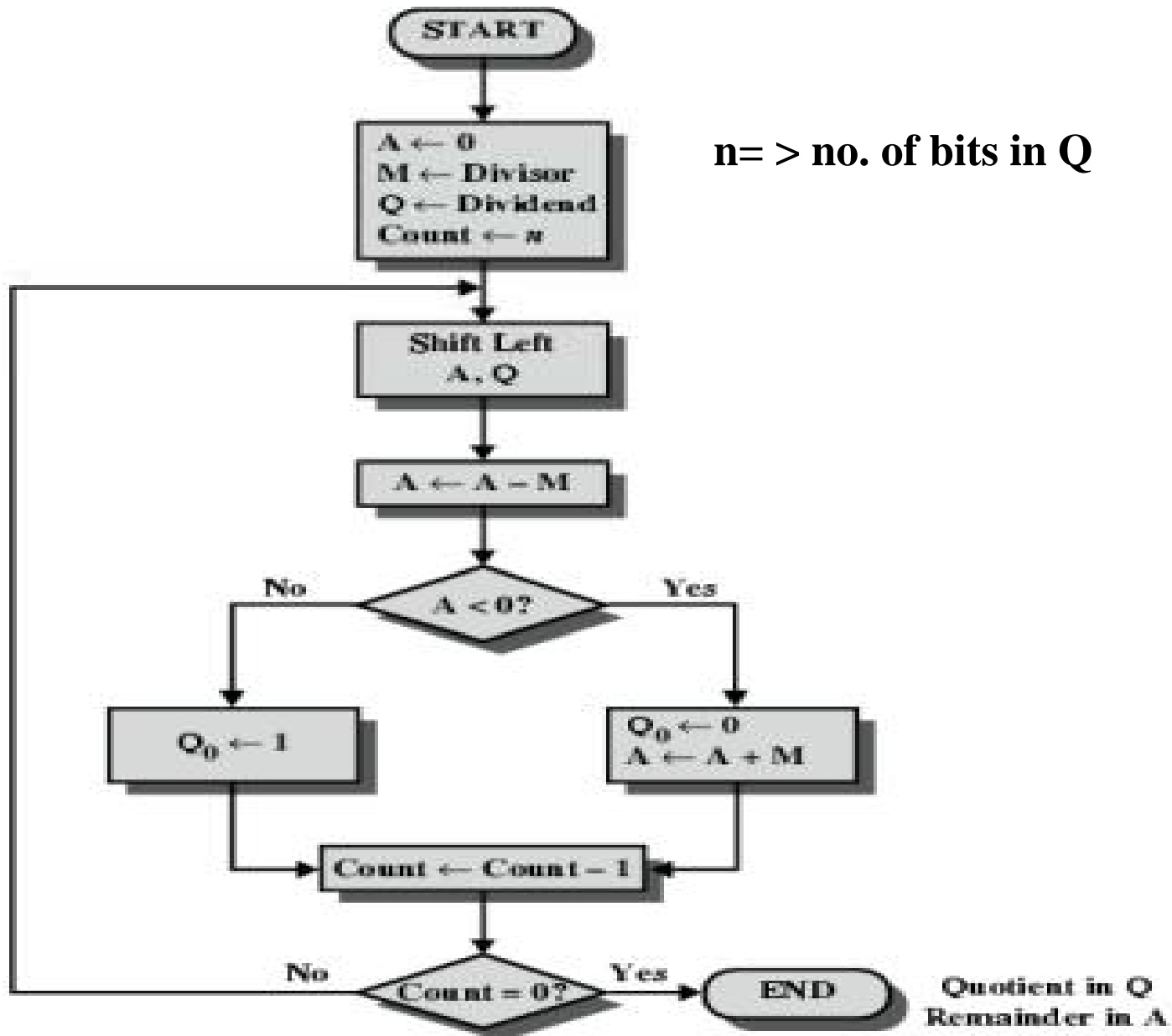

Non-Restoring Division Method

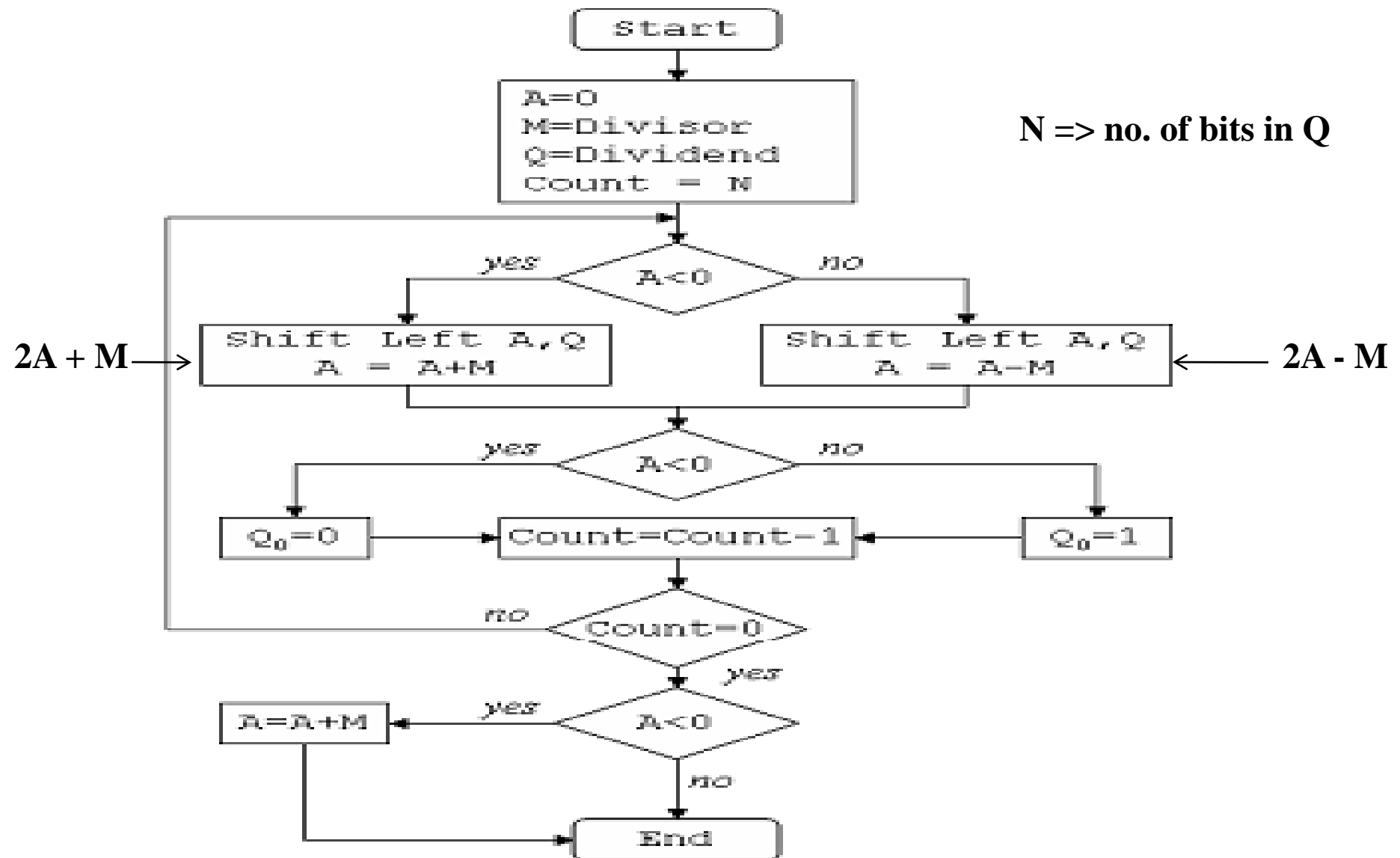



1. Sequential multiplier is for signed nos.
a) True b) False
2. Booth's multiplier is for signed nos.
a) True b) False
3. Restoring division method is for signed nos.
a) True b) False
4. Non-Restoring division method is for signed nos.
a) True b) False
5. For restoring division method, restoring of A is equivalent to-
a) $A \leftarrow A$ b) $A \leftarrow 2A$ c) $A \leftarrow A + M$ d) $A \leftarrow A - M$
6. Left-shift of A is Equivalent to –
a) A b) 2A c) $A + M$ d) $A - M$
7. For non-restoring division ,there will be no restoring operation -
a) True b) False
8. For Booth's multiplication , there will be no arithmetic operation when Q_0Q_{-1}
a) 00 & 10 b) 10 & 01 c) 00 & 11 d) 11 & 01

References

1. Computer Organization & Architecture – T. K. Ghosh
2. Computer System Architecture – M. Morris Mano

— *Thank You* —
Thank You